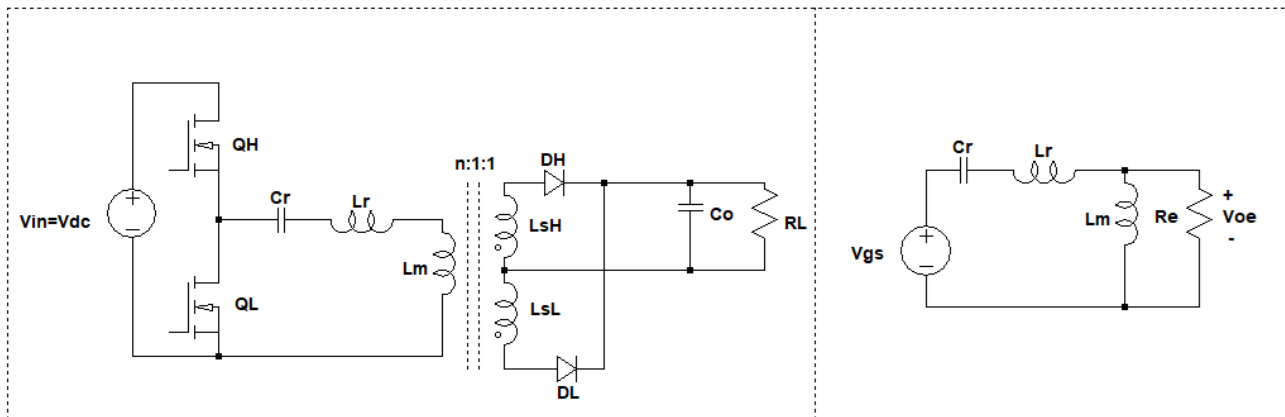


LLC tank pre-design calculations

Table of contents

- [Voltage Gain – Theoretical Overview](#)
- [Inputs and Specifications](#)
- [Transfo ratio and Voltage Gain](#)
- [Lm, Lr, Cr tank](#)
- [References](#)

Voltage Gain – Theoretical Overview



The voltage gain function (normalized) expression is:


$$M_g = \left| \frac{L_n \cdot f_n^2}{\left[(L_n + 1) \cdot f_n^2 - 1 \right] + j \left[(f_n^2 - 1) \cdot f_n \cdot Q_e \cdot L_n \right]} \right|$$

With:

$$L_n = \frac{L_m}{L_r}, \quad Q_e = \frac{\sqrt{\frac{L_r}{C_r}}}{R_e}, \quad f_n = \frac{f_{sw}}{f_0}, \quad f_0 = \frac{1}{2\pi \sqrt{L_r C_r}}$$

See page 3 formula (23) [\[1\]](#).

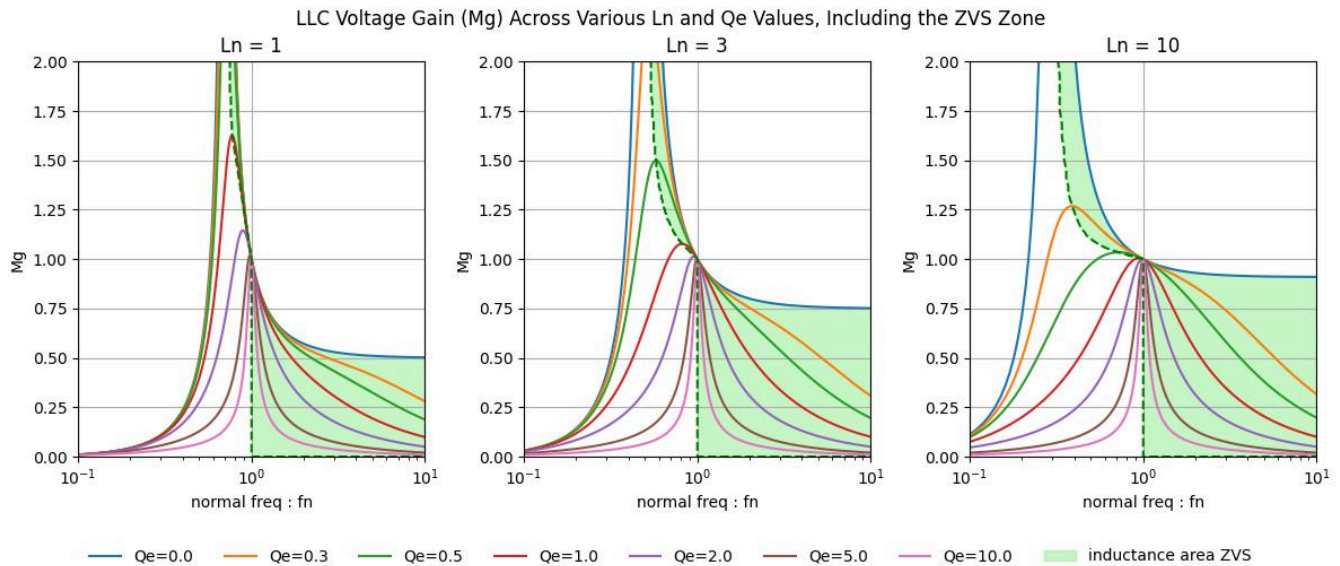You can found all formula of this chapeter in the same ref



Inputs and Specifications

$$\begin{aligned}
 V_{\ln_{\min}} &= 360 \text{ V} & V_{\ln_{\nom}} &= 380 \text{ V} & V_{\ln_{\max}} &= 400 \text{ V} \\
 V_{o_{\min}} &= 42 \text{ V} & V_{o_{\nom}} &= 48 \text{ V} & V_{o_{\max}} &= 54 \text{ V} \\
 \text{Power} &= 1200 \text{ W} & f_{\nom} &= 100000.000 \text{ Hz}
 \end{aligned}$$

Inputs data

```

{'V_In_min': 360.0,
 'V_In_nom': 380.0,
 'V_In_max': 400.0,
 'Vo_min': 42.0,
 'Vo_nom': 48.0,
 'Vo_max': 54.0,
 'Power': 1200.0,
 'f_nom': 100000.0}

```

Transfo ratio and Voltage Gain

$$n = \frac{V_{\ln_{\nom}}}{V_{o_{\nom}} \cdot 2} = \frac{380}{48 \cdot 2} = 3.958$$

Choose an integer value to simplify the transformer design.

$$n = \operatorname{round}(n) = \operatorname{round}(3.958) = 4$$

$$\begin{aligned} \mathrm{Vf} &= 0.200 \text{ V} \text{ (drop voltage in the mos)} \\ \mathrm{efficiency} &= 0.950 \text{ (hypothesis)} \\ \mathrm{loss} &= 1 - \mathrm{efficiency} = 1 - 0.950 = 0.050 \\ \mathrm{Io}_{nom} &= \frac{\mathrm{Power}}{\mathrm{Vo}_{nom}} = \frac{1200}{48} = 25.000 \text{ A} \\ V_{loss} &= \frac{\frac{\mathrm{Power}}{\mathrm{efficiency}}}{\frac{\mathrm{Power}}{\mathrm{Io}_{nom}}} = \frac{1200 \cdot 0.050}{0.950} = 2.526 \text{ V} \end{aligned}$$

$$\begin{aligned} \mathrm{margin} &= 0.010 \\ \mathrm{Mg}_{min} &= n \cdot \frac{\mathrm{Vo}_{min} \cdot \left(1 - \mathrm{margin} \right) + \mathrm{Vf}}{\frac{V_{ln_{max}}}{2}} = 4 \cdot \frac{42 \cdot \left(1 - 0.010 \right) + 0.200}{\frac{400}{2}} = 0.836 \\ \mathrm{Mg}_{max} &= n \cdot \frac{\mathrm{Vo}_{max} \cdot \left(1 + \mathrm{margin} \right) + \mathrm{Vf} + V_{loss}}{\frac{V_{ln_{min}}}{2}} = 4 \cdot \frac{54 \cdot \left(1 + 0.010 \right) + 0.200 + 2.526}{\frac{360}{2}} = 1.273 \\ \mathrm{Mg}_{max110} &= \mathrm{Mg}_{max} \cdot \left(\frac{110}{100} \right) = 1.273 \cdot \left(\frac{110}{100} \right) = 1.400 \end{aligned}$$

Lm, Lr, Cr tank

Below we will use grid search to find the best values for **Ln** and **Qe**.

The idea:

- Change **Ln** in the range: start = 1, stop = 10, step = 0.01 (around 100 points)
- Change **Qe** in the range: start = 0.1, stop = 1, step = 0.01 (around 10 points)

We will select the **Ln** and **Qe** values that give an **Mg** value closest to **Mg_max110**.

Top 6 (Ln, Qe) Combinations Matching **Mg_max110**


The following 6 values of **Ln** and **Qe** closely match the target voltage gain **Mg_max110**.

These rows were selected based on the criterion that **Mg_ape** is nearly equal to **Mg_max110**.

$$\mathrm{Mg}_{max110} = 1.400$$

	Lnc	Qec	Lm_uH	Lr_uH	Cr_nF	fn_min	fn_max	fsw_min	fsw_max	Mg_ape
0	2.41	0.64	61.127	25.364	99.867314	0.6375	1.3790	63750.0	137900.0	1.400142
1	3.00	0.55	65.392	21.797	116.209238	0.6017	1.5622	60170.0	156220.0	1.400062
2	3.46	0.50	68.562	19.816	127.830162	0.5707	1.7698	57070.0	176980.0	1.399923
3	3.68	0.48	70.005	19.023	133.156419	0.5471	1.9035	54710.0	190350.0	1.400284
4	4.21	0.44	73.413	17.438	145.261548	0.5324	2.4133	53240.0	241330.0	1.400277
5	4.71	0.41	76.532	16.249	155.890441	0.5077	3.6928	50770.0	369280.0	1.400231

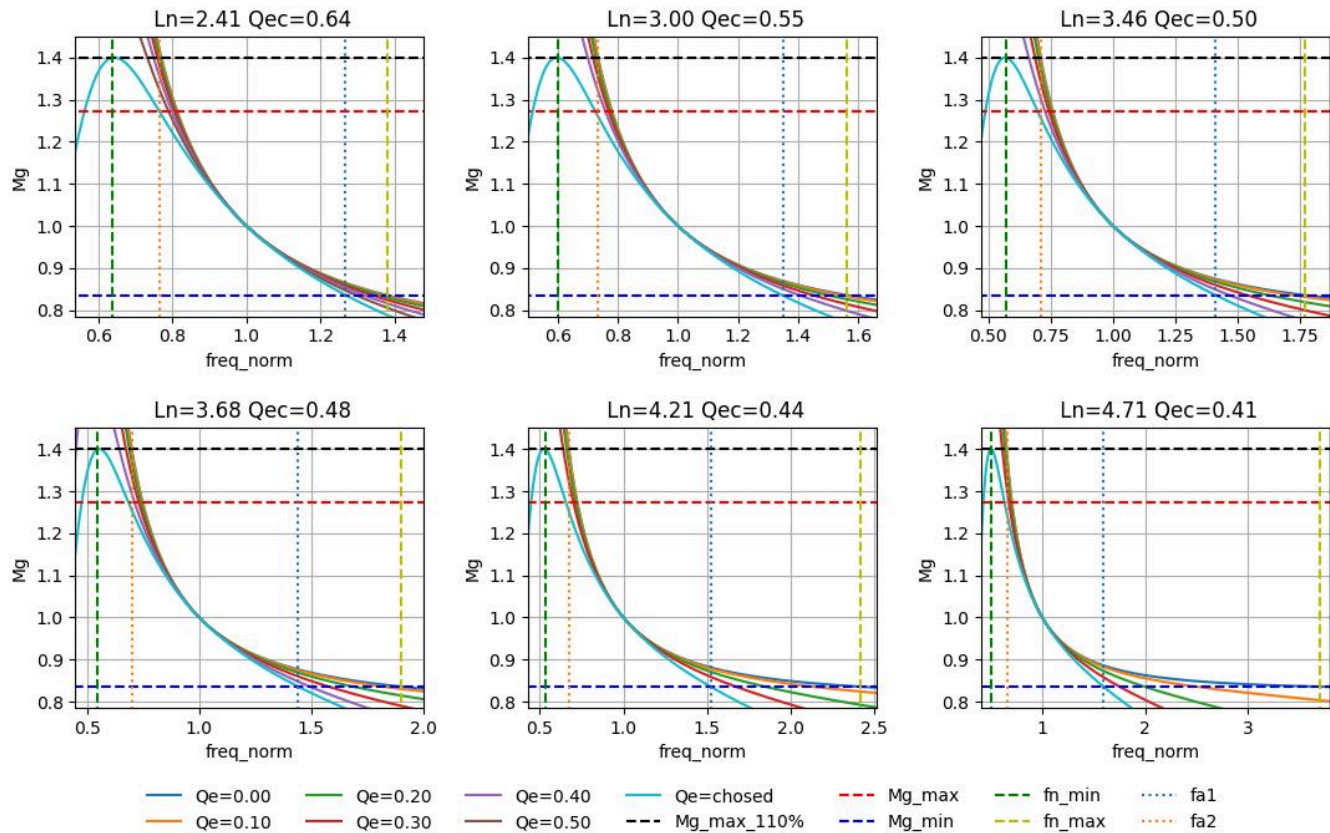Grid search for L_n and Q_e to find the best pair of values.



$$\begin{aligned} \mathrm{Lnc} \quad \&= 3 \quad \mathrm{Qec} \quad \&= 0.550 \end{aligned}$$


$L_n = 3$ and $Q_e = 0.55$ represent an optimal compromise due to the following:

- **Moderate gain slope ($\Delta M/\Delta f$):**

In the inductive region, the gain rises gradually with frequency, enabling stable control without abrupt sensitivity shifts.

- **Limited frequency span (f_{min} to f_{max}):**

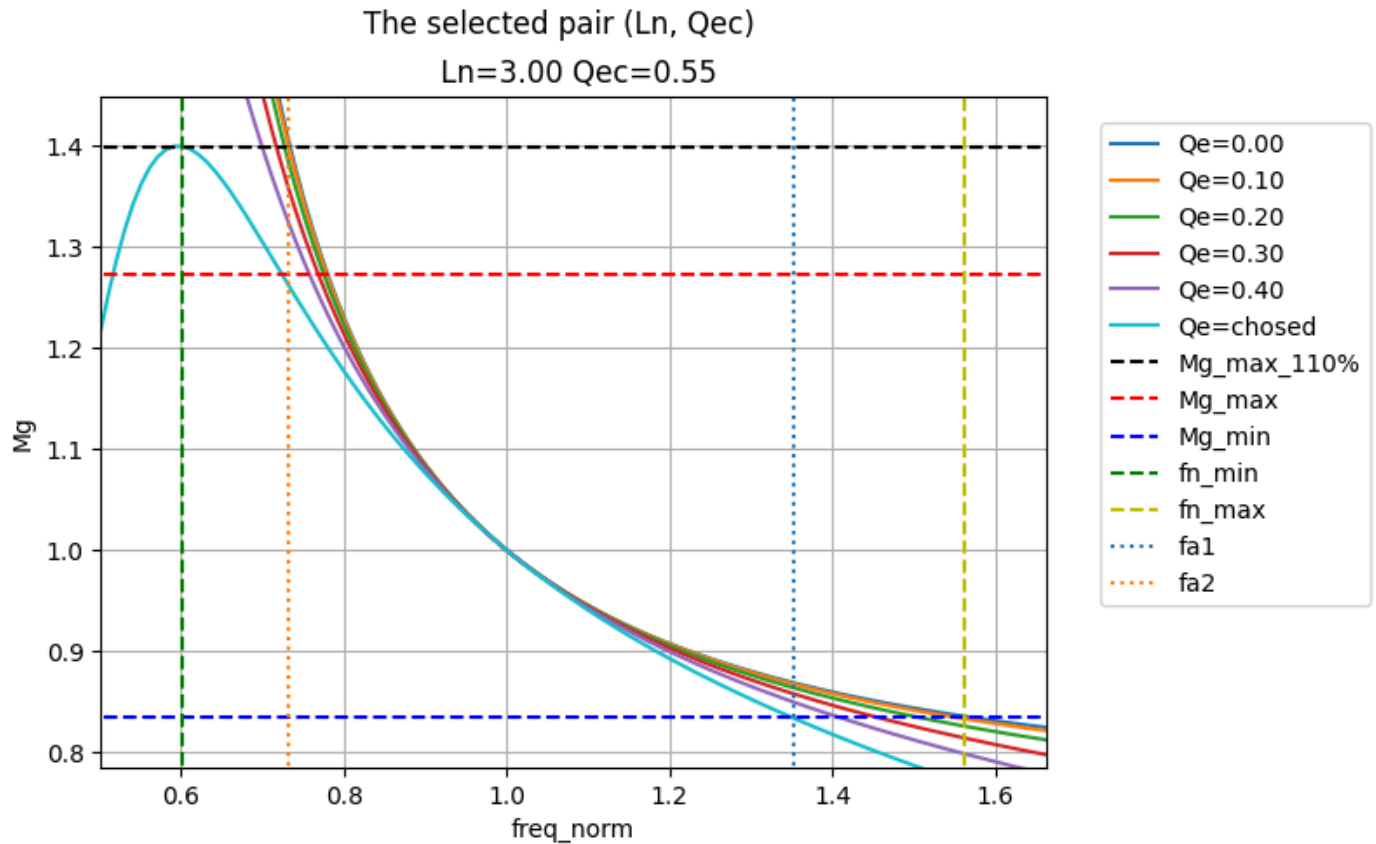These parameters restrict the switching frequency range, simplifying component design, controller implementation, and consistent ZVS operation.



Equivalent resistor

$$\begin{aligned} \mathrm{Re}_{\mathrm{nom}} &= 8 \cdot \left(n \right)^2 \cdot \frac{\mathrm{Vo}_{\mathrm{nom}}}{\left(\pi \right)^2 \cdot \mathrm{Io}_{\mathrm{nom}}} = 8 \cdot \left(4 \right)^2 \cdot \frac{48}{\left(3.142 \right)^2 \cdot 25.000} = 24.901 \\ \mathrm{Re}_{\mathrm{nom}} &= \operatorname{round} \left(\mathrm{Re}_{\mathrm{nom}} \right) \\ \mathrm{Re}_{110} &= \operatorname{round} \left(24.901, 3 \right) = 24.901 \\ \mathrm{Re}_{110} &= 8 \cdot \left(n \right)^2 \cdot \frac{\mathrm{Vo}_{\mathrm{nom}}}{\left(\pi \right)^2 \cdot \mathrm{Io}_{\mathrm{nom}} \cdot 1.1} = 8 \cdot \left(4 \right)^2 \cdot \frac{48}{\left(3.142 \right)^2 \cdot 25.000 \cdot 1.1} = 22.637 \\ P_{\mathrm{re}_{110}} &= \frac{\left(\frac{V_{\mathrm{Ln}_{\mathrm{nom}}}}{\left(\frac{380}{2} \right)^2 \cdot \mathrm{Re}_{110}} \right)^2}{\mathrm{Re}_{110}} = \frac{\left(\frac{380}{2} \right)^2}{24.901} = 1449.741 \end{aligned}$$

Lm, Lr, Cr values

$$\begin{aligned} \mathrm{Cr}_{nF} &= \frac{1 \times 10^9}{2 \cdot \pi \cdot \mathrm{Qec} \cdot f_{nom} \cdot \mathrm{Re}_{nom}} = \frac{1 \times 10^9}{2 \cdot 3.142 \cdot 0.550 \cdot 100000.000 \cdot 24.901} \\ &= 116.209 \text{ } \mathrm{Cr} \\ \left(\mathrm{Cr} \right)^{\frac{1}{3}} &= \left(116.209 \right)^{\frac{1}{3}} = 4.83 \\ \mathrm{Lr} &= \frac{1}{\left(2 \cdot \pi \cdot f_{nom} \right)^2 \cdot \mathrm{Cr}} \cdot 1 \times 10^{-9} = \frac{1}{\left(2 \cdot 3.142 \cdot 100000.000 \right)^2 \cdot 116.209} \cdot 1 \times 10^{-9} \\ &= 0.000 \text{ } \mathrm{Lr}_{uH} \\ \mathrm{Lr}_{uH} &= \mathrm{Lr} \cdot 1 \times 10^6 = 0.000 \cdot 1 \times 10^6 = 0.000 \text{ } \mathrm{Lr}_{uH} \\ \left(\mathrm{Lr}_{uH} \right)^{\frac{1}{3}} &= \left(0.000 \right)^{\frac{1}{3}} = 0.000 \text{ } \mathrm{Lm} \\ \mathrm{Lm} \cdot \mathrm{Lnc} &= 0.000 \cdot 3.000 = 0.000 \text{ } \mathrm{Lm}_{uH} \\ \mathrm{Lm}_{uH} \cdot 1 \times 10^6 &= 0.000 \cdot 1 \times 10^6 = 0.000 \text{ } \mathrm{Lm}_{uH} \end{aligned}$$

Verification

$$\begin{aligned} \mathrm{Qcal} &= \frac{\sqrt{\frac{\mathrm{Lr}}{\mathrm{Cr} \cdot 1 \times 10^{-9}}}}{\mathrm{Re}_{110} \cdot 1.1} = \frac{\sqrt{\frac{0.000}{116.209 \cdot 1 \times 10^{-9}}}}{22.637 \cdot 1.1} \\ &= 0.550 \text{ } \mathrm{Qec} = 0.550 \end{aligned}$$

Fsw limites and primary secondary currents

$$\begin{aligned} \mathrm{fsw}_{min} &= \left(\mathrm{fn}_{min} \cdot f_{nom} \right)^{\frac{1}{2}} = \left(0.602 \cdot 100000.000 \right)^{\frac{1}{2}} = 60170.000 \text{ } \mathrm{Hz} \\ \mathrm{fsw}_{max} &= \left(\mathrm{fn}_{max} \cdot f_{nom} \right)^{\frac{1}{2}} = \left(1.562 \cdot 100000.000 \right)^{\frac{1}{2}} = 156220.000 \text{ } \mathrm{Hz} \\ \mathrm{wmin} &= 2 \cdot \pi \cdot \mathrm{fsw}_{min} = 2 \cdot 3.142 \cdot 60170.000 = 378059.260 \text{ } \mathrm{rad/s} \\ \mathrm{wmax} &= 2 \cdot \pi \cdot \mathrm{fsw}_{max} = 2 \cdot 3.142 \cdot 156220.000 = 981559.209 \text{ } \mathrm{rad/s} \\ \mathrm{Im}_{rms} &= 2 \cdot \sqrt{2} \cdot n \cdot \frac{\mathrm{Vo}_{nom}}{\pi \cdot \mathrm{Lm} \cdot \mathrm{wmin}} = 2 \cdot \sqrt{2} \cdot 4 \cdot \frac{48}{3.142 \cdot 0.000 \cdot 378059.260} = 6.992 \text{ } \mathrm{Arms} \\ \mathrm{Io}_{rms} &= 1.1 \cdot \pi \cdot \frac{\mathrm{Io}}{n \cdot 2 \cdot \sqrt{2}} = 1.1 \cdot 3.142 \cdot \frac{25.000}{4 \cdot 2 \cdot \sqrt{2}} = 7.636 \text{ } \mathrm{Arms @ 110\%} \\ \mathrm{Irrms} &= \sqrt{\mathrm{Io}_{rms}^2 + \mathrm{Io}^2} = \sqrt{7.636^2 + 25.000^2} = 26.000 \text{ } \mathrm{Arms} \\ \mathrm{L}_{second_{uH}} &= \frac{\mathrm{Lm}_{uH}}{\left(n \right)^2} = \frac{65.392}{4^2} = 4.087 \text{ } \mathrm{uH} \end{aligned}$$

Output data

Output datas

Lnc	3.000000e+00
Qec	5.500000e-01
Cr_nF	1.162090e+02
n	4.000000e+00
Lr_uH	2.179700e+01
Lm_uH	6.539200e+01
fsw_min	6.017000e+04
fsw_max	1.562200e+05
Im_rms	6.992000e+00
Io	2.500000e+01
loe_rms	7.636000e+00
los_rms	3.054500e+01
Ir_rms	1.035400e+01
L_second_uH	4.087000e+00
Re_nom	2.490100e+01
Re_110	2.263700e+01
Cr	1.162090e-07
Lr	2.179700e-05
Lm	6.539200e-05

References

[1] Hong Huang, *Designing an LLC Resonant Half-Bridge Power Converter*. Available:
<https://bbs.dianyuan.com/upload/community/2013/12/01/1385867010-65563.pdf> [2]

Code [Python notebook used to make this PDF](#)