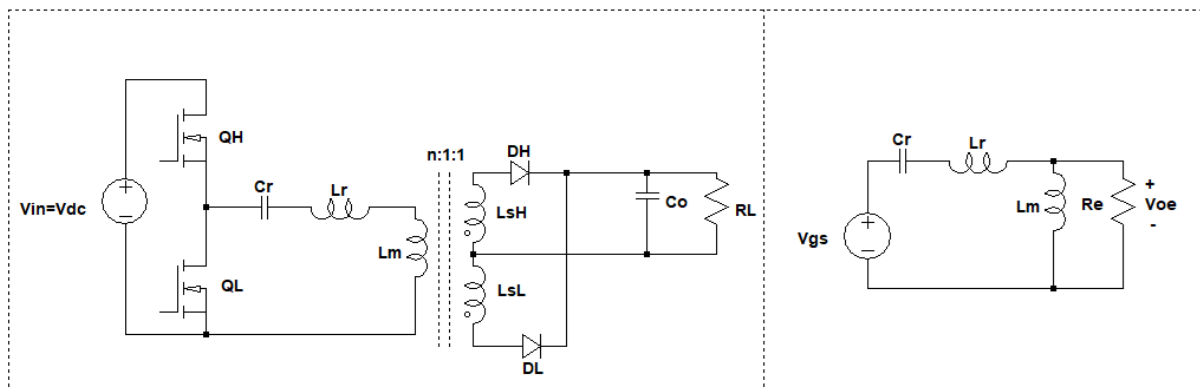


LLC tank pre-design calculations

Table of contents

- [Voltage Gain – Theoretical Overview](#)
- [Inputs and Specifications](#)
- [Transfo ratio and Voltage Gain](#)
- [Lm, Lr, Cr tank](#)
- [References](#)

Voltage Gain – Theoretical Overview



The voltage gain function (normalized) expression is:


$$M_g = \left| \frac{L_n \cdot f_n^2}{[(L_n + 1) \cdot f_n^2 - 1] + j[(f_n^2 - 1) \cdot f_n \cdot Q_e \cdot L_n]} \right|$$

With:

$$L_n = \frac{L_m}{L_r}, \quad Q_e = \frac{\sqrt{\frac{L_r}{C_r}}}{R_e}, \quad f_n = \frac{f_{sw}}{f_0}, \quad f_0 = \frac{1}{2\pi\sqrt{L_r C_r}}$$

See page 3 formula (23) [\[1\]](#).

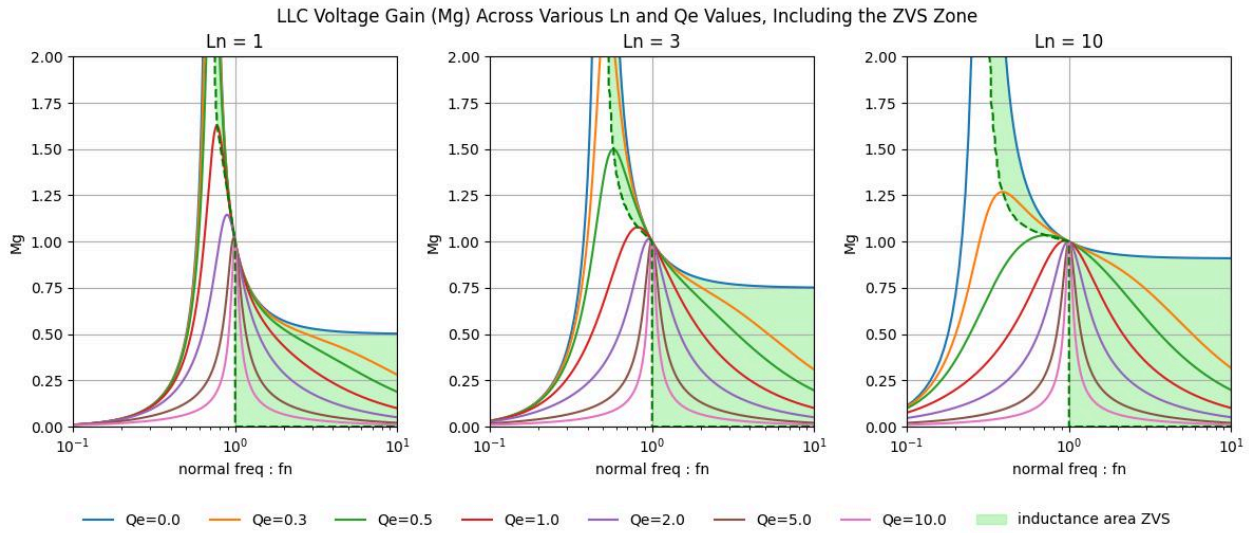You can found all formula of this chapeter in the same ref



Inputs and Specifications

$$V_{In_{min}} = 360 \text{ (v)}$$

$$V_{In_{nom}} = 380 \text{ (v)}$$

$$V_{In_{max}} = 400 \text{ (v)}$$

$$V_{O_{min}} = 42 \text{ (v)}$$

$$V_{O_{nom}} = 48 \text{ (v)}$$

$$V_{O_{max}} = 54 \text{ (v)}$$

$$\text{Power} = 1200 \text{ (w)}$$

$$f_{nom} = 100000.000 \text{ (Hz)}$$

Inputs data

```
{'V_In_min': 360.0,
'V_In_nom': 380.0,
'V_In_max': 400.0,
'Vo_min': 42.0,
'Vo_nom': 48.0,
'Vo_max': 54.0,
'Power': 1200.0,
'f_nom': 100000.0}
```

Transfo ratio and Voltage Gain

$$n = \frac{V_{In_{nom}}}{V_{O_{nom}} \cdot 2} = \frac{380}{48 \cdot 2} = 3.958$$

Choose an integer value to simplify the transformer design.

$$n = \text{round}(n) = \text{round}(3.958) = 4$$

$$V_f = 0.200 \text{ (drop voltage in the mos)}$$

$$\text{efficiency} = 0.950 \text{ (hypothesis)}$$

$$\text{loss} = 1 - \text{efficiency} = 1 - 0.950 = 0.050$$

$$I_{o_{nom}} = \frac{\text{Power}}{V_{o_{nom}}} = \frac{1200}{48} = 25.000 \text{ (A)}$$

$$V_{loss} = \frac{\frac{\text{Power} \cdot \text{loss}}{\text{efficiency}}}{I_{o_{nom}}} = \frac{\frac{1200 \cdot 0.050}{0.950}}{25.000} = 2.526 \text{ (v)}$$

$$\text{margin} = 0.010$$

$$Mg_{min} = n \cdot \frac{V_{o_{min}} \cdot (1 - \text{margin}) + V_f}{\frac{V_{In_{max}}}{2}} = 4 \cdot \frac{42 \cdot (1 - 0.010) + 0.200}{\frac{400}{2}} = 0.836$$

$$Mg_{max} = n \cdot \frac{V_{o_{max}} \cdot (1 + \text{margin}) + V_f + V_{loss}}{\frac{V_{In_{min}}}{2}} = 4 \cdot \frac{54 \cdot (1 + 0.010) + 0.200 + 2.526}{\frac{360}{2}} = 1.273$$

$$Mg_{max110} = Mg_{max} \cdot \left(\frac{110}{100} \right) = 1.273 \cdot \left(\frac{110}{100} \right) = 1.400$$

Lm, Lr, Cr tank

Below we will use grid search to find the best values for **Ln** and **Qe**.

The idea:

- Change **Ln** in the range: start = 1, stop = 10, step = 0.01 (around 100 points)
- Change **Qe** in the range: start = 0.1, stop = 1, step = 0.01 (around 10 points)

We will select the **Ln** and **Qe** values that give an **Mg** value closest to **Mg_max110**.

Top 6 (Ln, Qe) Combinations Matching **Mg_max110**


The following 6 values of **Ln** and **Qe** closely match the target voltage gain **Mg_max110**.

These rows were selected based on the criterion that **Mg_ape** is nearly equal to **Mg_max110**.

$$Mg_{max110} = 1.400$$

| | Lnc | Qec | Lm_uH | Lr_uH | Cr_nF | fn_min | fn_max | fsw_min | fsw_max | Mg_ape |
|---|------|------|--------|--------|------------|--------|--------|---------|----------|----------|
| 0 | 2.41 | 0.64 | 61.127 | 25.364 | 99.867314 | 0.6375 | 1.3790 | 63750.0 | 137900.0 | 1.400142 |
| 1 | 3.00 | 0.55 | 65.392 | 21.797 | 116.209238 | 0.6017 | 1.5622 | 60170.0 | 156220.0 | 1.400062 |
| 2 | 3.46 | 0.50 | 68.562 | 19.816 | 127.830162 | 0.5707 | 1.7698 | 57070.0 | 176980.0 | 1.399923 |
| 3 | 3.68 | 0.48 | 70.005 | 19.023 | 133.156419 | 0.5471 | 1.9035 | 54710.0 | 190350.0 | 1.400284 |
| 4 | 4.21 | 0.44 | 73.413 | 17.438 | 145.261548 | 0.5324 | 2.4133 | 53240.0 | 241330.0 | 1.400277 |
| 5 | 4.71 | 0.41 | 76.532 | 16.249 | 155.890441 | 0.5077 | 3.6928 | 50770.0 | 369280.0 | 1.400231 |

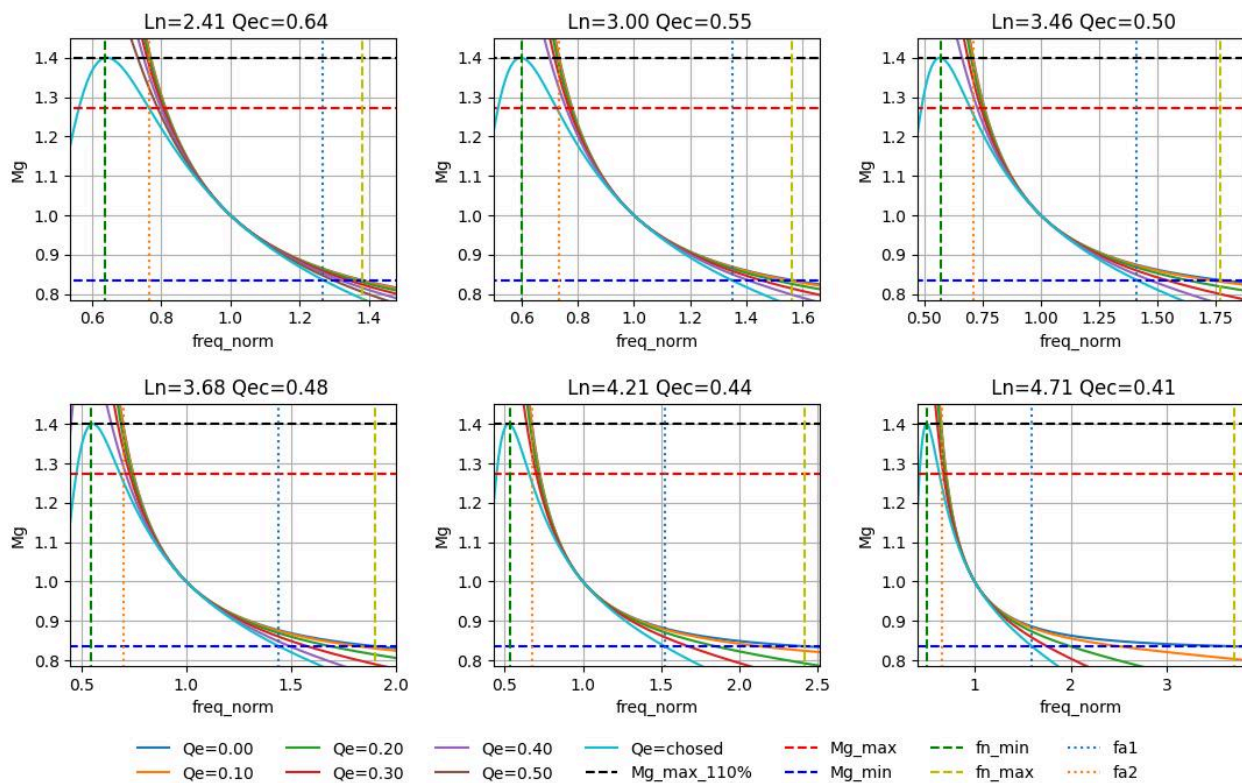Grid search for Ln and Qe to find the best pair of values.



$L_{nc} = 3$

$Q_{ec} = 0.550$

$L_{nc} = 3$ and $Q_{ec} = 0.55$ represent an optimal compromise due to the following:

- **Moderate gain slope ($\Delta M/\Delta f$):**

In the inductive region, the gain rises gradually with frequency, enabling stable control without abrupt sensitivity shifts.

- **Limited frequency span (f_{min} to f_{max}):**

These parameters restrict the switching frequency range, simplifying component design, controller implementation, and consistent ZVS operation.

Equivalent resistor

$$R_{e_{nom}} = 8 \cdot (n)^2 \cdot \frac{V_{o_{nom}}}{(\pi)^2 \cdot I_{o_{nom}}} = 8 \cdot (4)^2 \cdot \frac{48}{(3.142)^2 \cdot 25.000} = 24.901$$

$$R_{e_{nom}} = \text{round}(R_{e_{nom}}, 3) = \text{round}(24.901, 3) = 24.901$$

$$R_{e_{110}} = 8 \cdot (n)^2 \cdot \frac{V_{o_{nom}}}{(\pi)^2 \cdot I_{o_{nom}} \cdot 1.1} = 8 \cdot (4)^2 \cdot \frac{48}{(3.142)^2 \cdot 25.000 \cdot 1.1} = 22.637$$

$$P_{re_{110}} = \frac{\left(\frac{V_{In_{nom}}}{2}\right)^2}{R_{e_{nom}}} = \frac{\left(\frac{380}{2}\right)^2}{24.901} = 1449.741$$

Lm, Lr, Cr values

$$C_{r_{nF}} = \frac{1 \times 10^9}{2 \cdot \pi \cdot Q_{ec} \cdot f_{nom} \cdot R_{e_{nom}}} = \frac{1 \times 10^9}{2 \cdot 3.142 \cdot 0.550 \cdot 100000.000 \cdot 24.901} = 116.209 \text{ (nF)}$$

$$C_r = 116.209$$

$$C_r = \text{round}(C_r, 3) = \text{round}(116.209, 3) = 116.209$$

$$L_r = \frac{1}{(2 \cdot \pi \cdot f_{nom})^2 \cdot C_r \cdot 1 \times 10^{-9}} = \frac{1}{(2 \cdot 3.142 \cdot 100000.000)^2 \cdot 116.209 \cdot 1 \times 10^{-9}} = 0.000$$

$$L_{r_{uH}} = L_r \cdot 1 \times 10^6 = 0.000 \cdot 1 \times 10^6 = 21.797 \text{ (uH)}$$

$$L_{r_{uH}} = \text{round}(L_{r_{uH}}, 3) = \text{round}(21.797, 3) = 21.797$$

$$L_m = L_r \cdot L_{nc} = 0.000 \cdot 3 = 0.000$$

$$L_{m_{uH}} = L_m \cdot 1 \times 10^6 = 0.000 \cdot 1 \times 10^6 = 65.392 \text{ (uH)}$$



Verification

$$Q_{cal} = \frac{\sqrt{\frac{L_r}{C_r \cdot 1 \times 10^{-9}}}}{R_{e_{110}} \cdot 1.1} = \frac{\sqrt{\frac{0.000}{116.209 \cdot 1 \times 10^{-9}}}}{22.637 \cdot 1.1} = 0.550$$

$$Q_{ec} = 0.550$$

Fsw limites and primary secondary currents

$$fsw_{min} = \text{round}(fn_{min} \cdot f_{nom}, 2) = \text{round}(0.602 \cdot 100000.000, 2) = 60170.000 \text{ (Hz)}$$

$$fsw_{max} = \text{round}(fn_{max} \cdot f_{nom}, 2) = \text{round}(1.562 \cdot 100000.000, 2) = 156220.000 \text{ (Hz)}$$

$$wmin = 2 \cdot \pi \cdot fsw_{min} = 2 \cdot 3.142 \cdot 60170.000 = 378059.260 \text{ (rad/s)}$$

$$wmax = 2 \cdot \pi \cdot fsw_{max} = 2 \cdot 3.142 \cdot 156220.000 = 981559.209 \text{ (rad/s)}$$

$$Im_{rms} = 2 \cdot \sqrt{2} \cdot n \cdot \frac{Vo_{nom}}{\pi \cdot Lm \cdot wmin} = 2 \cdot \sqrt{2} \cdot 4 \cdot \frac{48}{3.142 \cdot 0.000 \cdot 378059.260} = 6.992 \text{ (Arms)}$$

$$Io = 25.000 \text{ (Arms)}$$

$$Ioe_{rms} = 1.1 \cdot \pi \cdot \frac{Io}{n \cdot 2 \cdot \sqrt{2}} = 1.1 \cdot 3.142 \cdot \frac{25.000}{4 \cdot 2 \cdot \sqrt{2}} = 7.636 \text{ (Arms @ 110\%)}$$

$$Ios_{rms} = Ioe_{rms} \cdot n = 7.636 \cdot 4 = 30.545 \text{ (Arms)}$$

$$Ir_{rms} = \sqrt{(Im_{rms})^2 + (Ioe)^2} = \sqrt{(6.992)^2 + (7.636)^2} = 10.354 \text{ (Arms)}$$

$$L_{second_{uH}} = \frac{Lm_{uH}}{(n)^2} = \frac{65.392}{(4)^2} = 4.087 \text{ (uH)}$$

Output data

```
{'Lnc': 3.0,
'Qec': 0.55,
'Cr_nF': 116.209,
'Lr_uH': 21.797,
'Lm_uH': 65.392,
'fsw_min': 60170.0,
'fsw_max': 156220.0,
'Im_rms': 6.992,
'Io': 25.0,
'Ioe_rms': 7.636,
'Ios_rms': 30.545,
'Ir_rms': 10.354,
'I_second_rms': 27.969,
'L_second_uH': 4.087,
'Re_nom': 24.901,
'Re_110': 22.637,
'Cr': 1.16209e-07,
'Lr': 2.1796999999999998e-05,
'Lm': 6.539199999999999e-05}
```

References

[1] Hong Huang, *Designing an LLC Resonant Half-Bridge Power Converter*. Available: <https://bbs.dianyuan.com/upload/community/2013/12/01/1385867010-65563.pdf>