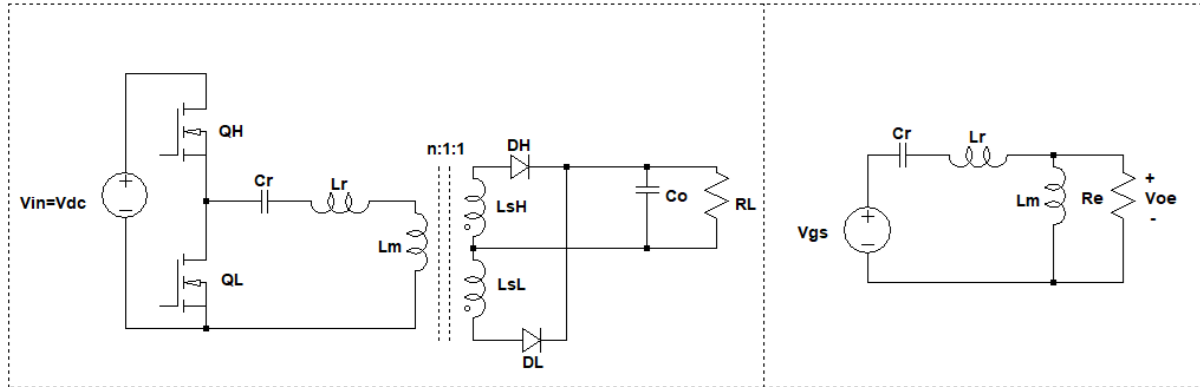


# LLC tank pre-design calculations

## Voltage Gain – Theoretical Overview



The voltage gain function (normalized) expression is:


$$M_g = \left| \frac{L_n \cdot f_n^2}{[(L_n + 1) \cdot f_n^2 - 1] + j[(f_n^2 - 1) \cdot f_n \cdot Q_e \cdot L_n]} \right|$$

With:

$$L_n = \frac{L_m}{L_r}, \quad Q_e = \frac{\sqrt{\frac{L_r}{C_r}}}{R_e}, \quad f_n = \frac{f_{sw}}{f_0}, \quad f_0 = \frac{1}{2\pi\sqrt{L_r C_r}}$$

See page 3 formula (23) [1].

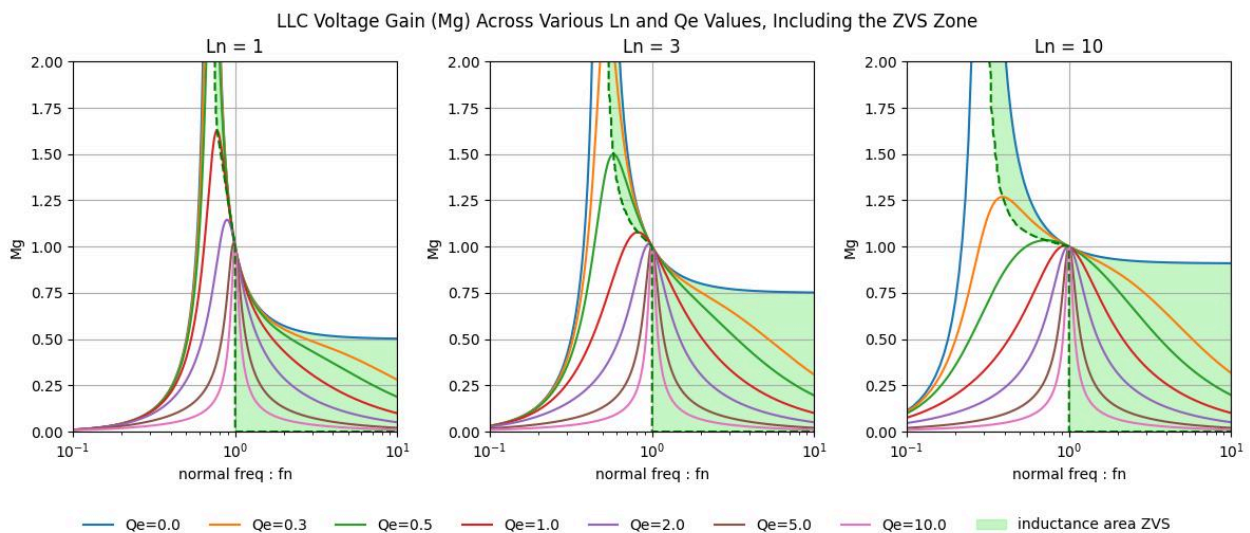You can found all formula of this chapter in the same ref



## Inputs and Specifications

$$V_{In_{min}} = 360 \text{ (v)}$$

$$V_{In_{nom}} = 380 \text{ (v)}$$

$$V_{In_{max}} = 400 \text{ (v)}$$

$$V_{O_{min}} = 42 \text{ (v)}$$

$$V_{O_{nom}} = 48 \text{ (v)}$$

$$V_{O_{max}} = 54 \text{ (v)}$$

$$\text{Power} = 1200 \text{ (w)}$$

$$f_{nom} = 100000.000 \text{ (Hz)}$$

### Inputs data

```
{'V_In_min': 360.0,
  'V_In_nom': 380.0,
  'V_In_max': 400.0,
  'Vo_min': 42.0,
  'Vo_nom': 48.0,
  'Vo_max': 54.0,
  'Power': 1200.0,
  'f_nom': 100000.0}
```

## Transfo ratio and Voltage Gain

$$n = \frac{V_{In_{nom}}}{V_{O_{nom}} \cdot 2} = \frac{380}{48 \cdot 2} = 3.958$$

Choose an integer value to simplify the transformer design.

$$n = \text{round}(n) = \text{round}(3.958) = 4$$

$$V_f = 0.200 \text{ (drop voltage in the mos)}$$

$$\text{efficiency} = 0.950 \text{ (hypothesis)}$$

$$\text{loss} = 1 - \text{efficiency} = 1 - 0.950 = 0.050$$

$$I_{O_{nom}} = \frac{\text{Power}}{V_{O_{nom}}} = \frac{1200}{48} = 25.000 \text{ (A)}$$

$$V_{loss} = \frac{\frac{\text{Power} \cdot \text{loss}}{\text{efficiency}}}{I_{O_{nom}}} = \frac{\frac{1200 \cdot 0.050}{0.950}}{25.000} = 2.526 \text{ (v)}$$

$$\text{margin} = 0.010$$

$$\text{Mg}_{min} = n \cdot \frac{V_{o_{min}} \cdot (1 - \text{margin}) + V_f}{\frac{V_{In_{max}}}{2}} = 4 \cdot \frac{42 \cdot (1 - 0.010) + 0.200}{\frac{400}{2}} = 0.836$$

$$\text{Mg}_{max} = n \cdot \frac{V_{o_{max}} \cdot (1 + \text{margin}) + V_f + V_{loss}}{\frac{V_{In_{min}}}{2}} = 4 \cdot \frac{54 \cdot (1 + 0.010) + 0.200 + 2.526}{\frac{360}{2}} = 1.273$$

$$\text{Mg}_{max110} = \text{Mg}_{max} \cdot \left(\frac{110}{100}\right) = 1.273 \cdot \left(\frac{110}{100}\right) = 1.400$$

## Lm, Lr, Cr tank

Below we will use grid search to find the best values for **Ln** and **Qe** .

**The idea:**

- Change **Ln** in the range: start = 1, stop = 10, step = 0.01 (around 100 points)
- Change **Qe** in the range: start = 0.1, stop = 1, step = 0.01 (around 10 points)

We will select the **Ln** and **Qe** values that give an **Mg** value closest to **Mg\_max110** .

### Top 6 (Ln, Qe) Combinations Matching **Mg\_max110**


The following 6 values of **Ln** and **Qe** closely match the target voltage gain **Mg\_max110** .

These rows were selected based on the criterion that **Mg\_ape** is nearly equal to **Mg\_max110** .

$$\text{Mg}_{max110} = 1.400$$

	Lnc	Qec	Lm_uH	Lr_uH	Cr_nF	fn_min	fn_max	fsw_min	fsw_max	Mg_ape
<b>0</b>	2.41	0.64	61.127	25.364	99.867314	0.6375	1.3790	63750.0	137900.0	1.400142
<b>1</b>	3.00	0.55	65.392	21.797	116.209238	0.6017	1.5622	60170.0	156220.0	1.400062
<b>2</b>	3.46	0.50	68.562	19.816	127.830162	0.5707	1.7698	57070.0	176980.0	1.399923
<b>3</b>	3.68	0.48	70.005	19.023	133.156419	0.5471	1.9035	54710.0	190350.0	1.400284
<b>4</b>	4.21	0.44	73.413	17.438	145.261548	0.5324	2.4133	53240.0	241330.0	1.400277
<b>5</b>	4.71	0.41	76.532	16.249	155.890441	0.5077	3.6928	50770.0	369280.0	1.400231

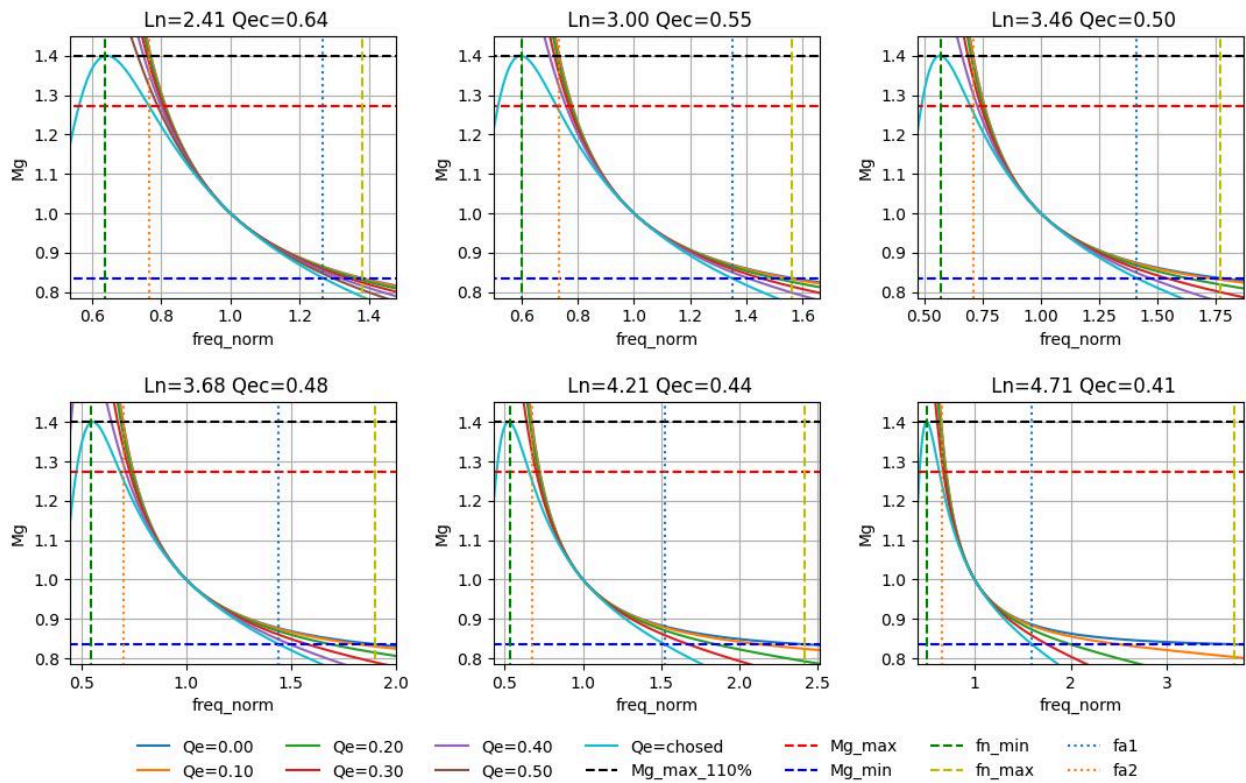Grid search for  $L_n$  and  $Q_e$  to find the best pair of values.



$$L_{nc} = 3$$

$$Q_{ec} = 0.550$$

$L_{nc} = 3$  and  $Q_{ec} = 0.55$  represent an optimal compromise due to the following:

- **Moderate gain slope ( $\Delta M/\Delta f$ ):**

In the inductive region, the gain rises gradually with frequency, enabling stable control without abrupt sensitivity shifts.

- **Limited frequency span ( $f_{\text{min}}$  to  $f_{\text{max}}$ ):**

These parameters restrict the switching frequency range, simplifying component design, controller implementation, and consistent ZVS operation.

## Equivalent resistor

$$Re_{nom} = 8 \cdot (n)^2 \cdot \frac{Vo_{nom}}{(\pi)^2 \cdot Io_{nom}} = 8 \cdot (4)^2 \cdot \frac{48}{(3.142)^2 \cdot 25.000} = 24.901$$

$$Re_{nom} = \text{round}(Re_{nom}, 3) = \text{round}(24.901, 3) = 24.901$$

$$Re_{110} = 8 \cdot (n)^2 \cdot \frac{Vo_{nom}}{(\pi)^2 \cdot Io_{nom} \cdot 1.1} = 8 \cdot (4)^2 \cdot \frac{48}{(3.142)^2 \cdot 25.000 \cdot 1.1} = 22.637$$

$$Pre_{110} = \frac{\left(\frac{Vin_{nom}}{2}\right)^2}{Re_{nom}} = \frac{\left(\frac{380}{2}\right)^2}{24.901} = 1449.741$$

## Lm, Lr, Cr values

$$Cr_{nF} = \frac{1 \times 10^9}{2 \cdot \pi \cdot Qec \cdot f_{nom} \cdot Re_{nom}} = \frac{1 \times 10^9}{2 \cdot 3.142 \cdot 0.550 \cdot 100000.000 \cdot 24.901} = 116.209 \text{ (nF)}$$

$$Cr = 116.209$$

$$Cr = \text{round}(Cr, 3) = \text{round}(116.209, 3) = 116.209$$

$$Lr = \frac{1}{(2 \cdot \pi \cdot f_{nom})^2 \cdot Cr \cdot 1 \times 10^{-9}} = \frac{1}{(2 \cdot 3.142 \cdot 100000.000)^2 \cdot 116.209 \cdot 1 \times 10^{-9}} = 0.000$$

$$Lr_{uH} = Lr \cdot 1 \times 10^6 = 0.000 \cdot 1 \times 10^6 = 21.797 \text{ (uH)}$$

$$Lr_{uH} = \text{round}(Lr_{uH}, 3) = \text{round}(21.797, 3) = 21.797$$

$$Lm = Lr \cdot Lnc = 0.000 \cdot 3 = 0.000$$

$$Lm_{uH} = Lm \cdot 1 \times 10^6 = 0.000 \cdot 1 \times 10^6 = 65.392 \text{ (uH)}$$



## Verification

$$Q_{cal} = \frac{\sqrt{\frac{Lr}{Cr \cdot 1 \times 10^{-9}}}}{Re_{110} \cdot 1.1} = \frac{\sqrt{\frac{0.000}{116.209 \cdot 1 \times 10^{-9}}}}{22.637 \cdot 1.1} = 0.550$$

$$Qec = 0.550$$

## Fsw limites and primary secondary currents

$$f_{sw_{min}} = \text{round}(f_{n_{min}} \cdot f_{nom}, 2) = \text{round}(0.602 \cdot 100000.000, 2) = 60170.000 \text{ (Hz)}$$

$$f_{sw_{max}} = \text{round}(f_{n_{max}} \cdot f_{nom}, 2) = \text{round}(1.562 \cdot 100000.000, 2) = 156220.000 \text{ (Hz)}$$

$$\omega_{min} = 2 \cdot \pi \cdot f_{sw_{min}} = 2 \cdot 3.142 \cdot 60170.000 = 378059.260 \text{ (rad/s)}$$

$$\omega_{max} = 2 \cdot \pi \cdot f_{sw_{max}} = 2 \cdot 3.142 \cdot 156220.000 = 981559.209 \text{ (rad/s)}$$

$$I_{m_{rms}} = 2 \cdot \sqrt{2} \cdot n \cdot \frac{V_{o_{nom}}}{\pi \cdot L_m \cdot \omega_{min}} = 2 \cdot \sqrt{2} \cdot 4 \cdot \frac{48}{3.142 \cdot 0.000 \cdot 378059.260} = 6.992 \text{ (Arms)}$$

$$I_o = 25.000 \text{ (Arms)}$$

$$I_{oe_{rms}} = 1.1 \cdot \pi \cdot \frac{I_o}{n \cdot 2 \cdot \sqrt{2}} = 1.1 \cdot 3.142 \cdot \frac{25.000}{4 \cdot 2 \cdot \sqrt{2}} = 7.636 \text{ (Arms @ 110\%)}$$

$$I_{os_{rms}} = I_{oe_{rms}} \cdot n = 7.636 \cdot 4 = 30.545 \text{ (Arms)}$$

$$I_{r_{rms}} = \sqrt{(I_{m_{rms}})^2 + (I_{oe})^2} = \sqrt{(6.992)^2 + (7.636)^2} = 10.354 \text{ (Arms)}$$

$$L_{second_{uH}} = \frac{L_{m_{uH}}}{(n)^2} = \frac{65.392}{(4)^2} = 4.087 \text{ (uH)}$$

## Output data

```
{'Lnc': 3.0,
'Qec': 0.55,
'Cr_nF': 116.209,
'Lr_uH': 21.797,
'Lm_uH': 65.392,
'fsw_min': 60170.0,
'fsw_max': 156220.0,
'Im_rms': 6.992,
'Io': 25.0,
'Ioe_rms': 7.636,
'Ios_rms': 30.545,
'Ir_rms': 10.354,
'I_second_rms': 27.969,
'L_second_uH': 4.087,
'Re_nom': 24.901,
'Re_110': 22.637}
```

## References

[1] Hong Huang, *Designing an LLC Resonant Half-Bridge Power Converter*. Available: <https://bbs.dianyuan.com/upload/community/2013/12/01/1385867010-65563.pdf>