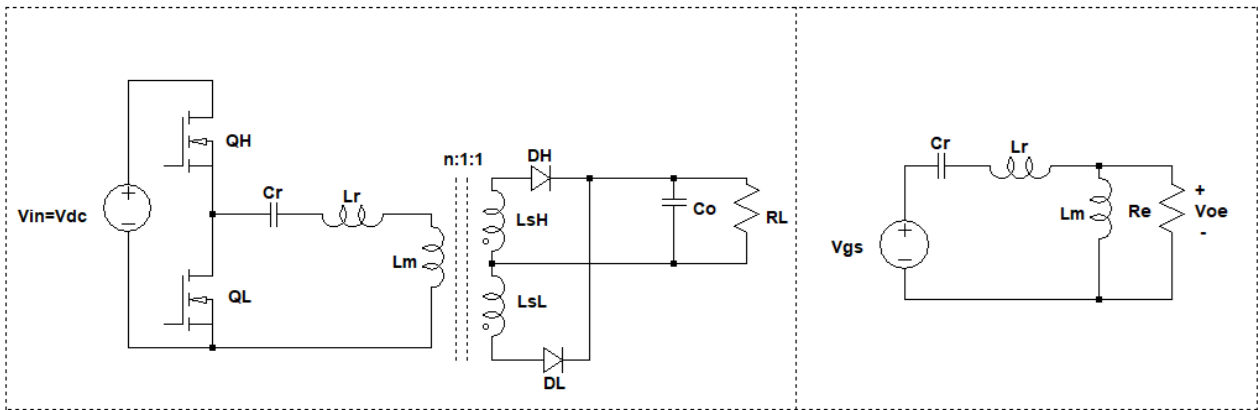


# LLC tank pre-design calculations

## Table of contents

- [Voltage Gain – Theoretical Overview](#)
- [Inputs and Specifications](#)
- [Transfo ratio and Voltage Gain](#)
- [Lm, Lr, Cr tank](#)
- [Simulation](#)
- [References](#)

## Voltage Gain – Theoretical Overview



**Figure 1:** The simplified schematic and the equivalent small-signal AC model

The voltage gain function (normalized) expression is:


$$M_g = \left| \frac{L_n \cdot f_n^2}{[(L_n + 1) \cdot f_n^2 - 1] + j[(f_n^2 - 1) \cdot f_n \cdot Q_e \cdot L_n]} \right|$$

With:

$$L_n = \frac{L_m}{L_r}, \quad Q_e = \frac{\sqrt{\frac{L_r}{C_r}}}{R_e}, \quad f_n = \frac{f_{sw}}{f_0}, \quad f_0 = \frac{1}{2\pi\sqrt{L_r C_r}}$$

See page 3 formula (23) [\[1\]](#).

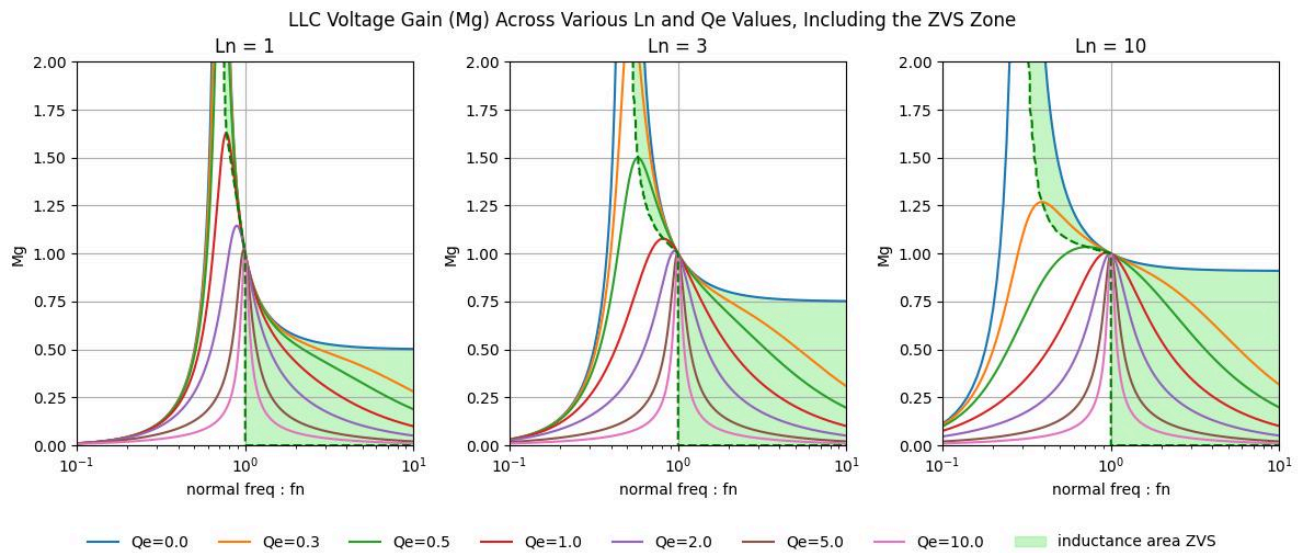You can found all formula of this chapeter in the same ref



## Inputs and Specifications

$$V_{In_{min}} = 360 \text{ (v)}$$

$$V_{In_{nom}} = 380 \text{ (v)}$$

$$V_{In_{max}} = 400 \text{ (v)}$$

$$V_{O_{min}} = 42 \text{ (v)}$$

$$V_{O_{nom}} = 48 \text{ (v)}$$

$$V_{O_{max}} = 54 \text{ (v)}$$

$$\text{Power} = 1200 \text{ (w)}$$

$$f_{nom} = 100000.000 \text{ (Hz)}$$

### Inputs data

```
{'V_In_min': 360.0,
'V_In_nom': 380.0,
'V_In_max': 400.0,
'Vo_min': 42.0,
'Vo_nom': 48.0,
'Vo_max': 54.0,
'Power': 1200.0,
'f_nom': 100000.0}
```

## Transfo ratio and Voltage Gain

$$n = \frac{V_{In_{nom}}}{V_{O_{nom}} \cdot 2} = \frac{380}{48 \cdot 2} = 3.958$$

Choose an integer value to simplify the transformer design.

$$n = \text{round}(n) = \text{round}(4) = 4$$

$$V_f = 0.200 \text{ (drop voltage in the mos)}$$

$$\text{efficiency} = 0.950 \text{ (hypothesis)}$$

$$\text{loss} = 1 - \text{efficiency} = 1 - 0.950 = 0.050$$

$$I_{o_{nom}} = \frac{\text{Power}}{V_{o_{nom}}} = \frac{1200}{48} = 25.000 \text{ (A)}$$

$$V_{loss} = \frac{\frac{\text{Power} \cdot \text{loss}}{\text{efficiency}}}{I_{o_{nom}}} = \frac{\frac{1200 \cdot 0.050}{0.950}}{25.000} = 2.526 \text{ (v)}$$

$$\text{margin} = 0.010$$

$$\begin{aligned} Mg_{min} &= n \cdot \frac{V_{o_{min}} \cdot (1 - \text{margin}) + V_f}{\frac{V_{In_{max}}}{2}} \\ &= 4 \cdot \frac{42 \cdot (1 - 0.010) + 0.200}{\frac{400}{2}} \\ &= 0.836 \end{aligned}$$

$$\begin{aligned} Mg_{max} &= n \cdot \frac{V_{o_{max}} \cdot (1 + \text{margin}) + V_f + V_{loss}}{\frac{V_{In_{min}}}{2}} \\ &= 4 \cdot \frac{54 \cdot (1 + 0.010) + 0.200 + 2.526}{\frac{360}{2}} \\ &= 1.273 \end{aligned}$$

$$\begin{aligned} Mg_{max110} &= Mg_{max} \cdot \left( \frac{110}{100} \right) \\ &= 1.273 \cdot \left( \frac{110}{100} \right) \\ &= 1.400 \end{aligned}$$

## Lm, Lr, Cr tank

Below we will use grid search to find the best values for **Ln** and **Qe**.

### The idea:

- Change **Ln** in the range: start = 1, stop = 10, step = 0.01 (around 100 points)
- Change **Qe** in the range: start = 0.1, stop = 1, step = 0.01 (around 10 points)

We will select the **Ln** and **Qe** values that give an **Mg** value closest to **Mg\_max110**.

## Top 6 (Ln, Qe) Combinations Matching $Mg_{max110}$


The following 6 values of  $Ln$  and  $Qe$  closely match the target voltage gain  $Mg_{max110}$ .

These rows were selected based on the criterion that  $Mg_{ape}$  is nearly equal to  $Mg_{max110}$ .

$$Mg_{max110} = 1.400$$

|   | Lnc  | Qec  | Lm_uH  | Lr_uH  | Cr_nF      | fn_min | fn_max | fsw_min | fsw_max  | Mg_ape   |
|---|------|------|--------|--------|------------|--------|--------|---------|----------|----------|
| 0 | 2.41 | 0.64 | 61.127 | 25.364 | 99.867314  | 0.6375 | 1.3790 | 63750.0 | 137900.0 | 1.400142 |
| 1 | 3.00 | 0.55 | 65.392 | 21.797 | 116.209238 | 0.6017 | 1.5622 | 60170.0 | 156220.0 | 1.400062 |
| 2 | 3.46 | 0.50 | 68.562 | 19.816 | 127.830162 | 0.5707 | 1.7698 | 57070.0 | 176980.0 | 1.399923 |
| 3 | 3.68 | 0.48 | 70.005 | 19.023 | 133.156419 | 0.5471 | 1.9035 | 54710.0 | 190350.0 | 1.400284 |
| 4 | 4.21 | 0.44 | 73.413 | 17.438 | 145.261548 | 0.5324 | 2.4133 | 53240.0 | 241330.0 | 1.400277 |
| 5 | 4.71 | 0.41 | 76.532 | 16.249 | 155.890441 | 0.5077 | 3.6928 | 50770.0 | 369280.0 | 1.400231 |

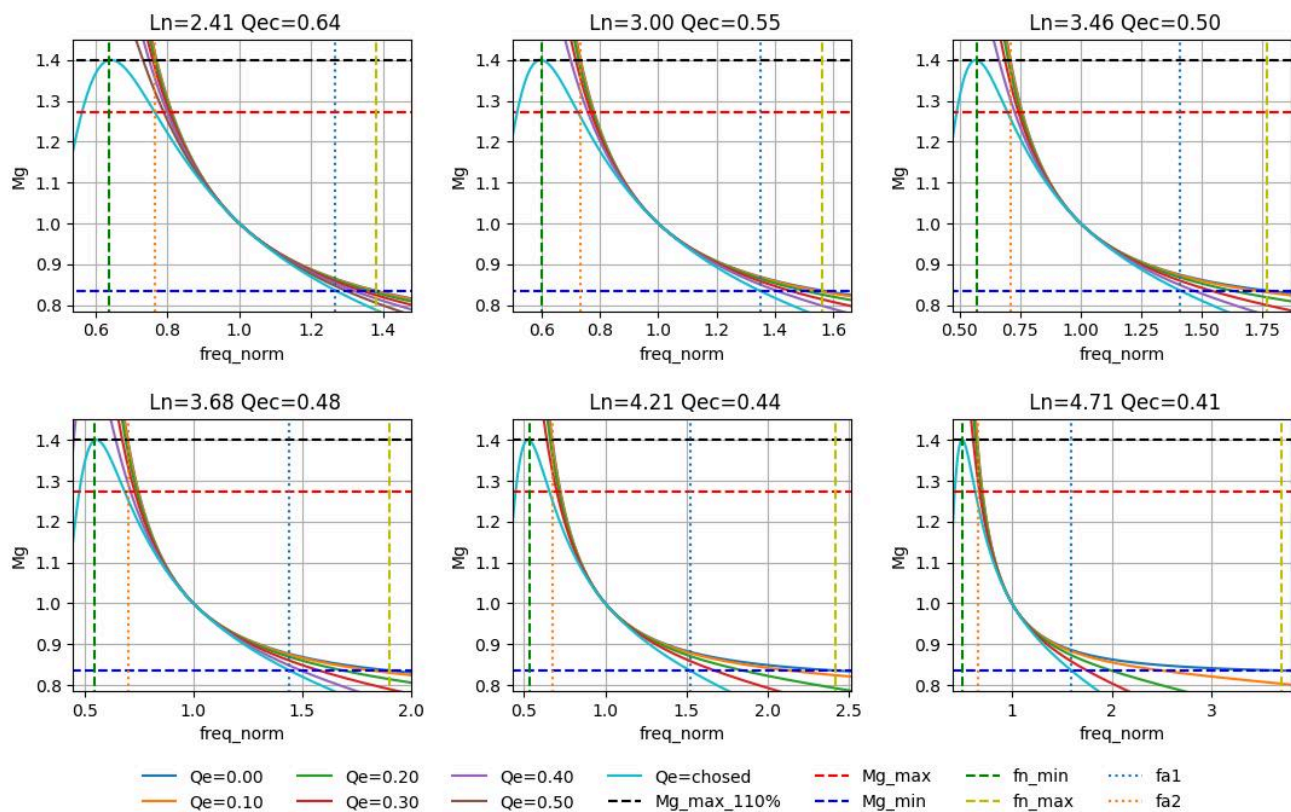Grid search for  $Ln$  and  $Qe$  to find the best pair of values.



$$Lnc = 3$$

$$Qec = 0.550$$


$Lnc = 3$  and  $Qec = 0.55$  represent an optimal compromise due to the following:

- Moderate gain slope ( $\Delta M/\Delta f$ ):**

In the inductive region, the gain rises gradually with frequency, enabling stable control without abrupt sensitivity shifts.

- **Limited frequency span ( $f_{\min}$  to  $f_{\max}$ ):**

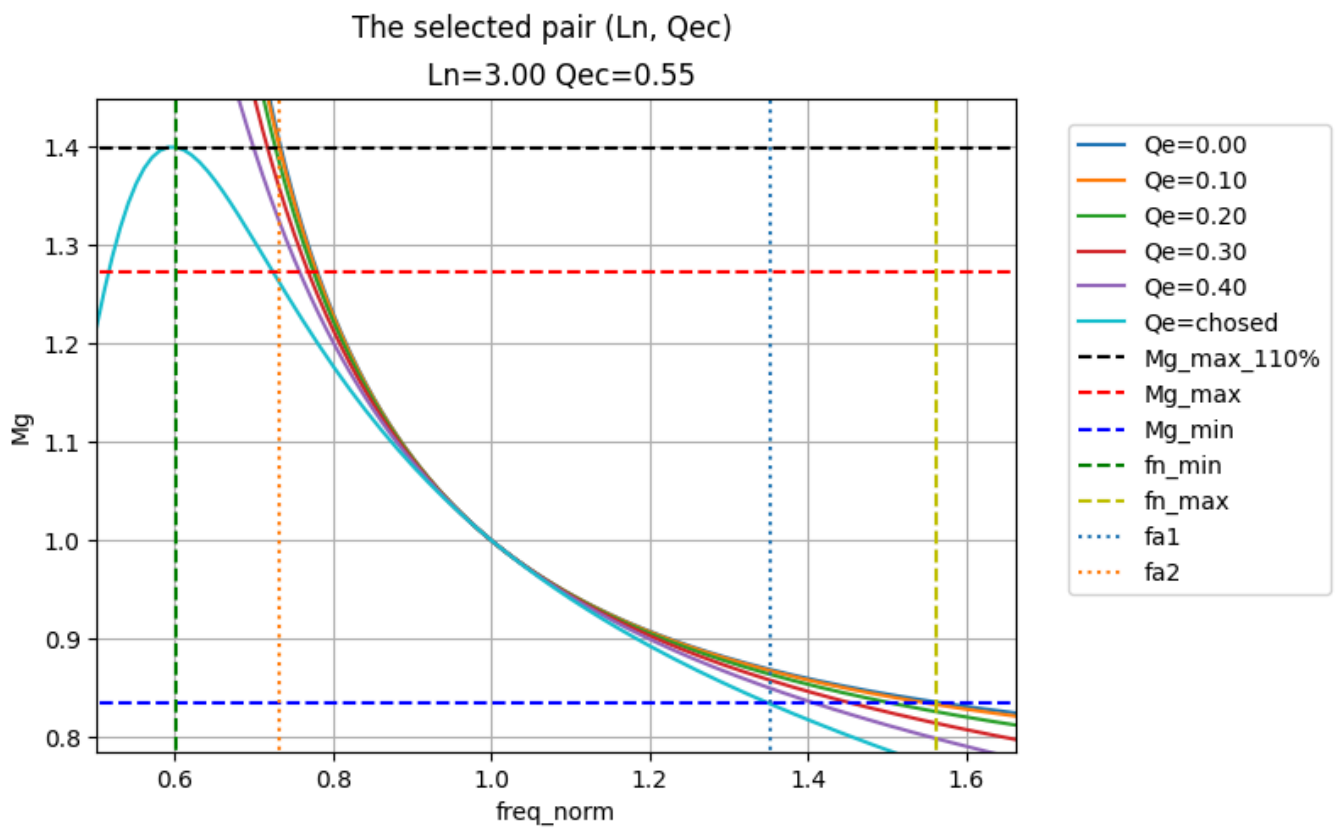These parameters restrict the switching frequency range, simplifying component design, controller implementation, and consistent ZVS operation.



Equivalent resistor

$$\begin{aligned}
\text{Re}_{nom} &= 8 \cdot (n)^2 \cdot \frac{V_{o_{nom}}}{(\pi)^2 \cdot I_{o_{nom}}} \\
&= 8 \cdot (4)^2 \cdot \frac{48}{(3.142)^2 \cdot 25.000} \\
&= 24.901
\end{aligned}$$

$$\begin{aligned}
\text{Re}_{nom} &= \text{round}(\text{Re}_{nom}, 3) \\
&= \text{round}(24.901, 3) \\
&= 24.901
\end{aligned}$$

$$\begin{aligned}
\text{Re}_{110} &= 8 \cdot (n)^2 \cdot \frac{V_{o_{nom}}}{(\pi)^2 \cdot I_{o_{nom}} \cdot 1.1} \\
&= 8 \cdot (4)^2 \cdot \frac{48}{(3.142)^2 \cdot 25.000 \cdot 1.1} \\
&= 22.637
\end{aligned}$$

$$\begin{aligned}
P_{re_{110}} &= \frac{\left(\frac{V_{Innom}}{2}\right)^2}{\text{Re}_{nom}} \\
&= \frac{\left(\frac{380}{2}\right)^2}{24.901} \\
&= 1449.741
\end{aligned}$$

## Lm, Lr, Cr values

$$\begin{aligned}
\text{Cr}_{nF} &= \frac{1 \times 10^9}{2 \cdot \pi \cdot Q_{ec} \cdot f_{nom} \cdot \text{Re}_{nom}} \\
&= \frac{1 \times 10^9}{2 \cdot 3.142 \cdot 0.550 \cdot 100000.000 \cdot 24.901} \\
&= 116.209 \text{ (nF)}
\end{aligned}$$

$$\text{Cr} = 116.209$$

$$\begin{aligned}
\text{Cr} &= \text{round}(\text{Cr}, 3) \\
&= \text{round}(116.209, 3) \\
&= 116.209
\end{aligned}$$

$$\begin{aligned}
L_r &= \frac{1}{(2 \cdot \pi \cdot f_{nom})^2 \cdot Cr \cdot 1 \times 10^{-9}} \\
&= \frac{1}{(2 \cdot 3.142 \cdot 100000.000)^2 \cdot 116.209 \cdot 1 \times 10^{-9}} \\
&= 0.000
\end{aligned}$$

$$\begin{aligned}
L_{r_{uH}} &= L_r \cdot 1 \times 10^6 \\
&= 0.000 \cdot 1 \times 10^6 \\
&= 21.797 \text{ (uH)}
\end{aligned}$$

$$\begin{aligned}
L_{r_{uH}} &= \text{round}(L_{r_{uH}}, 3) \\
&= \text{round}(21.797, 3) \\
&= 21.797
\end{aligned}$$

$$\begin{aligned}
L_m &= L_r \cdot L_{nc} \\
&= 0.000 \cdot 3.000 \\
&= 0.000
\end{aligned}$$

$$\begin{aligned}
L_{m_{uH}} &= L_m \cdot 1 \times 10^6 \\
&= 0.000 \cdot 1 \times 10^6 \\
&= 65.392 \text{ (uH)}
\end{aligned}$$

$$\begin{aligned}
L_{second_{uH}} &= \frac{L_{m_{uH}}}{(n)^2} \\
&= \frac{65.392}{(4)^2} \\
&= 4.087 \text{ (uH)}
\end{aligned}$$

### Verification

$$Q_{cal} = \frac{\sqrt{\frac{L_r}{Cr \cdot 1 \times 10^{-9}}}}{Re_{110} \cdot 1.1} = \frac{\sqrt{\frac{0.000}{116.209 \cdot 1 \times 10^{-9}}}}{22.637 \cdot 1.1} = 0.550$$

$$Q_{ec} = 0.550$$

### Fsw limites and primary secondary currents

$$\begin{aligned}
f_{sw_{min}} &= f_{n_{min}} \cdot f_{nom} \\
&= 0.602 \cdot 100000.000 \\
&= 60170.000 \text{ (Hz)}
\end{aligned}$$

$$\begin{aligned}
f_{sw_{max}} &= f_{n_{max}} \cdot f_{nom} \\
&= 1.562 \cdot 100000.000 \\
&= 156220.000 \text{ (Hz)}
\end{aligned}$$

$$\begin{aligned}
w_{min} &= 2 \cdot \pi \cdot f_{sw_{min}} \\
&= 2 \cdot 3.142 \cdot 60170.000 \\
&= 378059.260 \text{ (rad/s)}
\end{aligned}$$

$$\begin{aligned}
w_{max} &= 2 \cdot \pi \cdot f_{sw_{max}} \\
&= 2 \cdot 3.142 \cdot 156220.000 \\
&= 981559.209 \text{ (rad/s)}
\end{aligned}$$

$$\begin{aligned}
I_{m_{rms}} &= 2 \cdot \sqrt{2} \cdot n \cdot \frac{V_{o_{nom}}}{\pi \cdot L_m \cdot w_{min}} \\
&= 2 \cdot \sqrt{2} \cdot 4 \cdot \frac{48}{3.142 \cdot 0.000 \cdot 378059.260} \\
&= 6.992 \text{ (Arms)}
\end{aligned}$$

$$I_o = 25.000 \text{ (Arms)}$$

$$\begin{aligned}
I_{oe_{rms}} &= 1.1 \cdot \pi \cdot \frac{I_o}{n \cdot 2 \cdot \sqrt{2}} \\
&= 1.1 \cdot 3.142 \cdot \frac{25.000}{4 \cdot 2 \cdot \sqrt{2}} \\
&= 7.636 \text{ (Arms @ 110\%)}
\end{aligned}$$

$$\begin{aligned}
I_{os_{rms}} &= I_{oe_{rms}} \cdot n \\
&= 7.636 \cdot 4 \\
&= 30.545 \text{ (Arms)}
\end{aligned}$$

$$\begin{aligned}
I_{r_{rms}} &= \sqrt{(I_{m_{rms}})^2 + (I_{oe})^2} \\
&= \sqrt{(6.992)^2 + (7.636)^2} \\
&= 10.354 \text{ (Arms)}
\end{aligned}$$


**Output data**



```
{'Lnc': 3.0,
'Qec': 0.55,
'Cr_nF': 116.209,
'n': 4.0,
'Lr_uH': 21.797,
'Lm_uH': 65.392,
'fsw_min': 60170.0,
'fsw_max': 156220.0,
'Im_rms': 6.992,
'Io': 25.0,
'Ioe_rms': 7.636,
'Ios_rms': 30.545,
'Ir_rms': 10.354,
'L_second_uH': 4.087,
'Re_nom': 24.901,
'Re_110': 22.637,
'Cr': 1.16209e-07,
'Lr': 2.1796999999999998e-05,
'Lm': 6.539199999999999e-05}
```

## Simulations

### AC simulation of the LLC gain

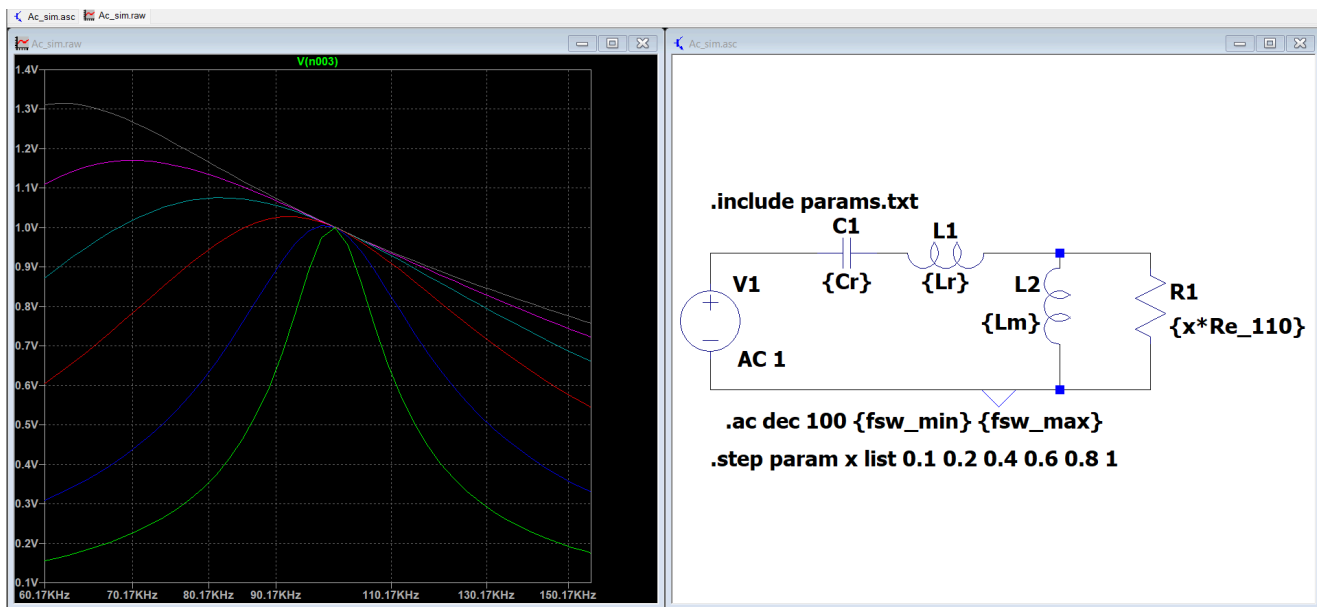


**Figure 2:** AC response of the LLC tank, for load is 10, 20, 40, 60, 80 and 100% of  $Re_{110}$

The frequency response is close to our calculated target for frequencies in the range  $[F_{min}, F_{max}]$ .

[you can download the simulation file here](#)

### Simple simulation (nominal)

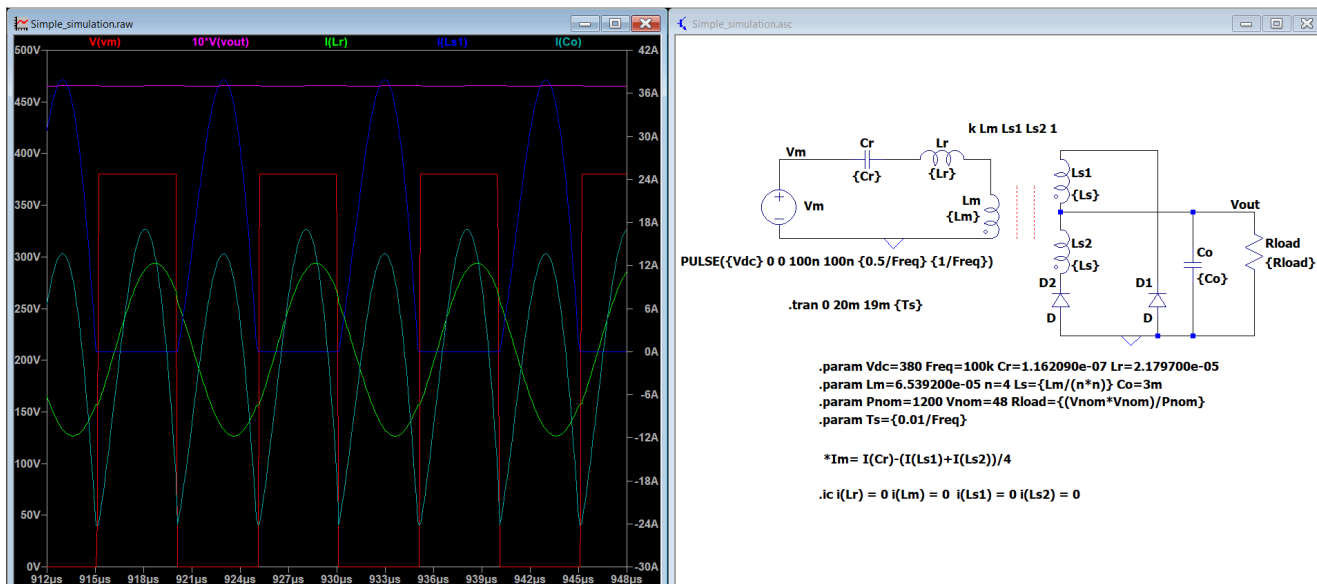

**Figure 3:** The simulation of the LLC tank

The output is around 48V for an input of 380V and 100kHz (nominal).  
The  $L_m$  current is close to a sine wave form as expected (resonance).

[you can download the simulation file here](#)

## References

- [1] Hong Huang, *Designing an LLC Resonant Half-Bridge Power Converter*. Available: <https://bbs.dianyuan.com/upload/community/2013/12/01/1385867010-65563.pdf> [2]  
Code [Python notebook](#) used to make this PDF